



FPGA PROJECT


VHDL components:

1. **Instruction Fetch:** This component accesses program memory, retrieves the current instruction, and updates the program counter.
2. **Instruction Decoder:** Responsible for interpreting the instruction and generating various control signals based on the instruction type (R, I, or J).
3. **Execution Unit:** Handles arithmetic and logical operations specified by the decoded instruction.
4. **Control Unit:** Manages the control signals, configuring them based on the instruction type (R, I, or J).
5. **Memory Interface (MEM):** Interfaces with external memory to load and store data.
6. **Write-Back Unit:** Records the computation result in RAM memory.
7. **UART (Universal Asynchronous Receiver-Transmitter):** Facilitates data transmission between the FPGA board and a computer.

Additional resources

- + FPGA board (preferable Spartan3E because of the constraints);
- + Cable to connect the FPGA board to the computer;


Project outline

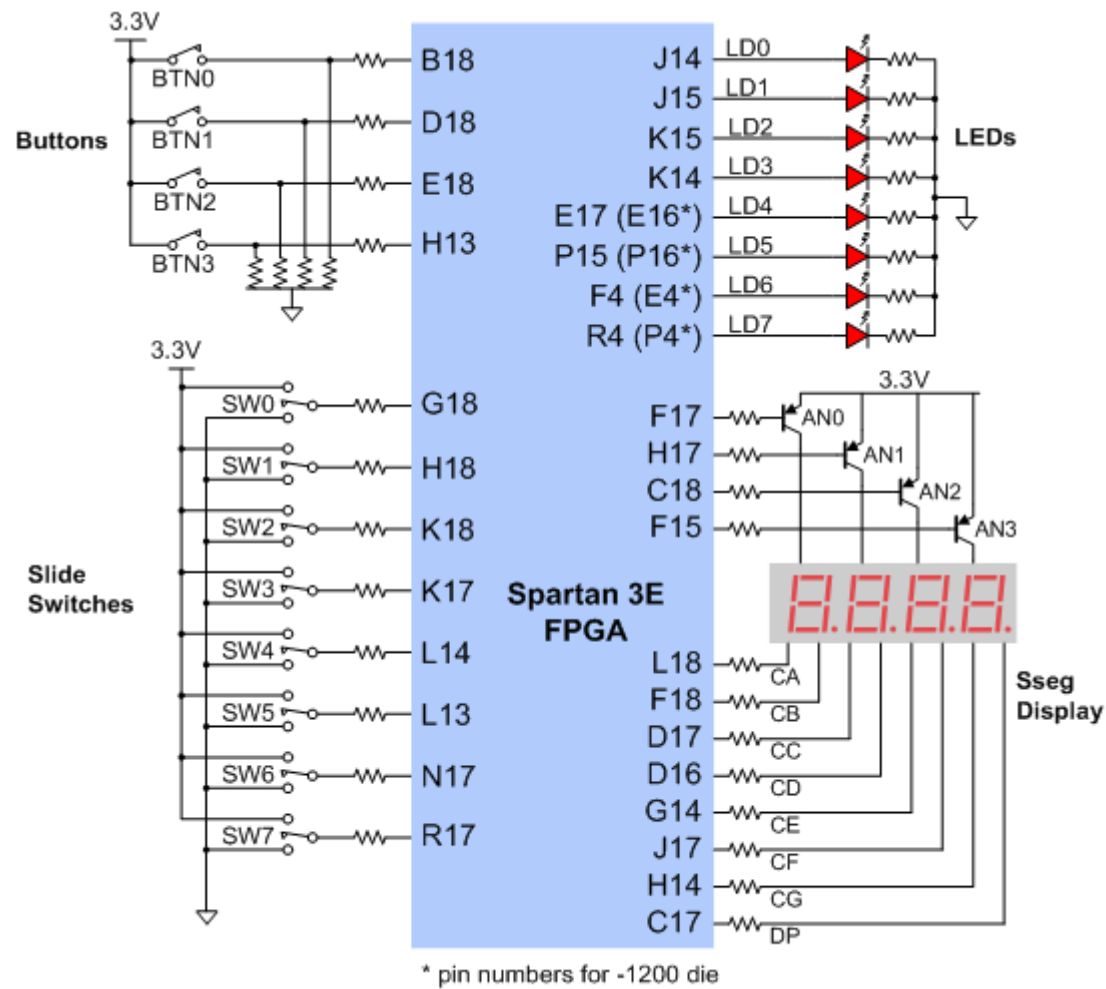

* pin numbers for -1200 die

PROJECT CALCULATION

1. STATUS CODING

 

2. STATE DIAGRAM

STARI ACTUALE			STARI VIITOARE			IESIRI				BISTABIL JK					
Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	Y_3	Y_2	Y_1	Y_0	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	0	\bar{a}	a	0	0	0	0	0	x	\bar{a}	x	a	x
0	0	1	a	\bar{a}	1	1	0	0	0	a	x	\bar{a}	x	x	0
0	1	0	0	0	0	0	1	1	1	0	x	x	1	0	x
0	1	1	1	1	b	1	1	0	0	1	x	x	0	x	\bar{b}
1	0	0	1	\bar{b}	b	1	0	1	0	x	0	\bar{b}	x	b	x
1	0	1	0	1	0	1	1	1	0	x	1	1	x	x	1
1	1	0	1	0	0	0	1	1	0	x	0	x	1	0	x
1	1	1	1	0	1	1	1	0	1	x	0	x	0	x	0

3. CALCULATION OF BISTABLE FUNCTIONS JK

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	0	0	x	x
1	a	1	x	x

$$J_2 = a * \overline{Q_2} * Q_0 + Q_1 * Q_0$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	x	x	0	0
1	x	x	0	1

$$K_2 = \overline{Q_1} * Q_0$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	\bar{a}	x	x	\bar{b}
1	\bar{a}	x	x	1

$$J_1 = \bar{a} * \overline{Q_2} + \bar{b} * Q_2 + Q_2 * Q_0$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	x	1	1	x
1	x	0	0	x

$$K_1 = \overline{Q_0}$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	a	0	0	b
1	x	x	x	x

$$J_0 = a * \overline{Q_1} * \overline{Q_2} + b * Q_2 * \overline{Q_1}$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	x	x	x	x
1	0	\bar{b}	0	1

$$K_0 = \bar{b} * Q_1 * \overline{Q_2} + \overline{Q_1} * Q_2$$

4. OUTPUTS CALCULATION

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	0	0	0	1
1	1	1	1	1

$$Y_3 = Q_2 * \overline{Q_1} + Q_0$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	0	1	1	0
1	0	1	1	1

$$Y_2 = Q_1 + Q_0 * Q_1$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	0	1	1	1
1	0	0	0	1

$$Y_1 = \overline{Q_0} * Q_1 + \overline{Q_1} * Q_2 + \overline{Q_0} * Q_2$$

$Q_0 \backslash Q_2, Q_1$	00	01	11	10
0	0	1	0	0
1	0	0	1	0

$$Y_0 = \overline{Q_0} * \overline{Q_2} * Q_1 + Q_1 * Q_2 * Q_0$$